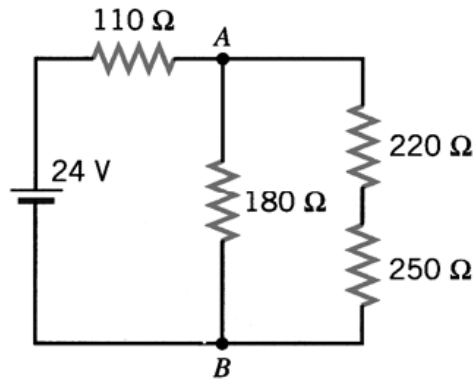


Combination Circuits

Often an electric circuit is wired partially in series and partially in parallel. The key to determining the current, voltage, and power in such a case is to deal with the circuit in parts, with the resistances in each part being in series or parallel with each other.

Example 1

The diagram below shows a circuit composed of a 24 V battery and four resistors, whose resistances are $110\ \Omega$, $180\ \Omega$, $220\ \Omega$, and $250\ \Omega$. Find




- the total current supplied by the battery.
- the voltage between points A and B in the circuit.


Circuits Worksheet #7

1. In each of the following diagrams, determine the equivalent resistance between points A and B.


a) ($99.8\ \Omega$)

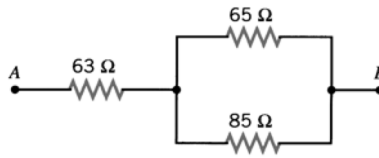


b) ($6.76\ \Omega$)

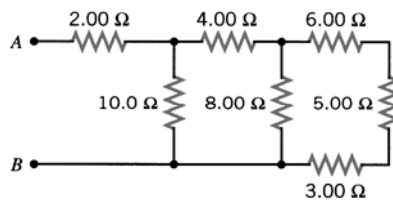

c) ($4.60\ \Omega$)

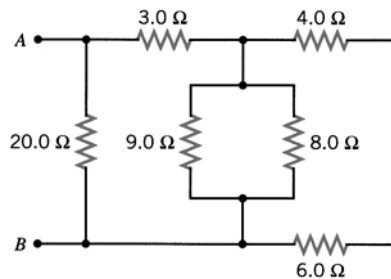

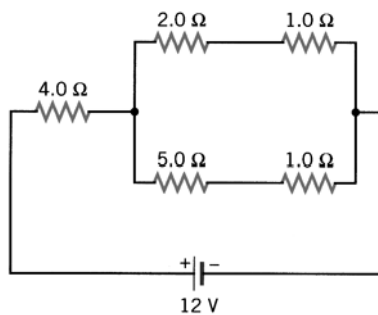2. Determine the power dissipated in the $5.0\ \Omega$ resistor in the circuit shown in the drawing.
($2.2\ W$)



3. The current in the $8.00\ \Omega$ resistor in the drawing is 0.5 A . Find the current in (a) the $20.0\ \Omega$ resistor and in (b) the $9.00\ \Omega$ resistor. (0.75 A , 2.11 A)

