

Circuits Worksheet #8

1. A $16\ \Omega$ and a $8\ \Omega$ resistor are connected in parallel. Find the equivalent resistance. ($5.33\ \Omega$)

2. A $5\ \Omega$, $10\ \Omega$, and $15\ \Omega$ resistor are connected in parallel.
 - a) Find the equivalent resistance. ($2.73\ \Omega$)
 - b) Find the current drawn by each resistor when they are connected in parallel to a $6\ V$ battery. ($1.2\ A$, $0.6\ A$, $0.4\ A$)
 - c) Find the total current drawn by the three resistors by adding the currents in part b. Show that a single resistor of resistance equal to the value in part a draws the same amount of current from the $6\ V$ battery. ($2.2\ A$)


3. The following three appliances are connected in parallel to a $120\ V$ house circuit; a $1600\ W$ toaster; a $1250\ W$ microwave; and a $600\ W$ coffee pot. If all three were operated at the same time, what total current would they draw? ($28.75\ A$)

4. Three resistors connected in parallel have individual resistances of $450\ \Omega$, $1350\ \Omega$, and $2700\ \Omega$. If the circuit is connected to a $40\ V$ source, find
 - a) the current through each resistor. ($0.0889\ A$, $0.0296\ A$, $0.0148\ A$)
 - b) the total current delivered by the source. ($0.133\ A$)
 - c) the equivalent resistance of the circuit. ($300\ \Omega$)
 - d) the rate at which the source delivers energy. ($5.33\ W$)
 - e) the rate of heat dissipation in each resistor. ($3.56\ W$, $1.19\ W$, $0.593\ W$)

5. Given that the resistors R_1 , R_2 , and R_3 are wired in parallel to a voltage source, complete the table:

Component	Current	Voltage	Resistance	Power
Source		$75\ V$		
R_1				$37.5\ W$
R_2				$12.5\ W$
R_3				$4.69\ W$

6. For the circuit shown below,

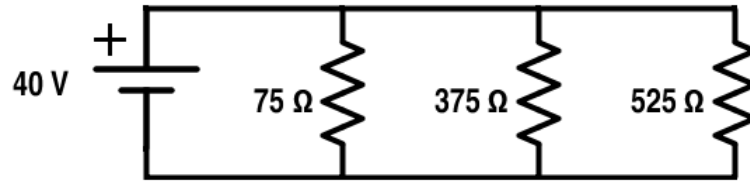

determine:


- the equivalent resistance of the circuit. (55.9Ω)
 - the current through each resistor. ($0.533 A$, $0.106 A$, $0.0762 A$)
 - the total current delivered by the source. ($0.716 A$)
 - the power delivered by the source. ($28.6 W$)
 - the power dissipated in each resistor. ($21.33 W$, $4.27 W$, $3.05 W$)
7. Given that the resistors R_1 , R_2 , and R_3 are wired in parallel to a voltage source, complete the table:

Component	Current	Voltage	Resistance	Power
Source		120 V		
R_1			1250 Ω	
R_2	0.032 A			
R_3				1.28 W

8. Given that the resistors R_1 , R_2 , and R_3 are wired in parallel to a voltage source, complete the table:

Component	Current	Voltage	Resistance	Power
Source				0.3715 W
R_1		0.16 V		
R_2			0.275 Ω	
R_3	0.286 A			


9. For the circuit shown below,

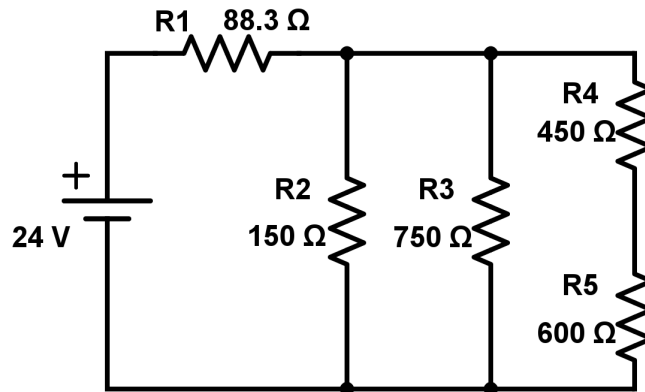

determine:


- a) the equivalent resistance of the circuit. (200Ω)
- b) the total current drawn by the resistors. ($0.12 A$)
- c) the potential drop across the parallel combination. ($13.4 V$)
- d) the current through resistors R_2 , R_3 , and R_4 . ($0.0894 A$, $0.0179 A$, $0.0128 A$)
- e) the power delivered by the source. ($2.88 W$)

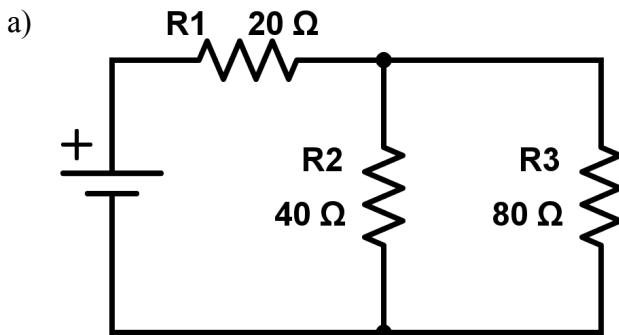10. Determine the equivalent resistance of each of the following combinations of resistors.




Answer : 46.7Ω

b)

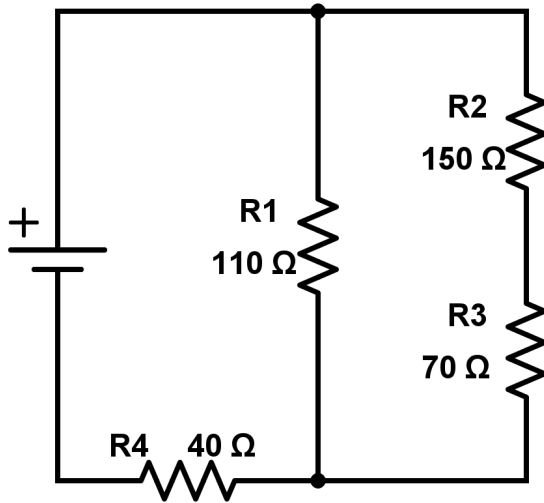


Answer : 113 Ω

c)

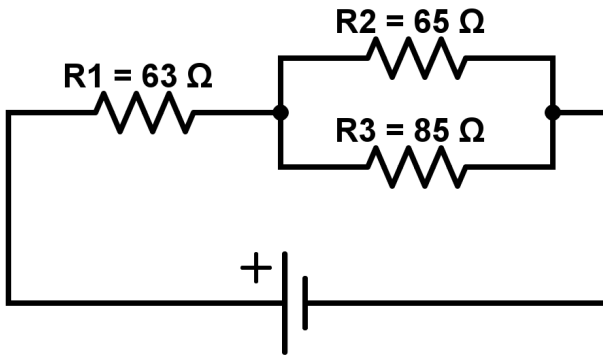

Answer : 99.8 Ω

d)

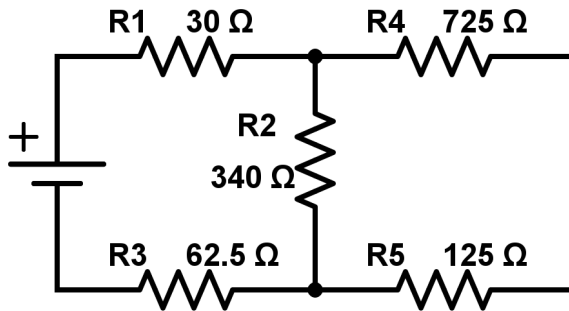

Answer : 335 Ω

Answers for problems 5, 7, and 8:

Component	Current	Voltage	Resistance	Power
Source	0.729 A	75 V		54.7 W
R_1	0.500 A	75 V	150 Ω	37.5 W
R_2	0.167 A	75 V	450 Ω	12.5 W
R_3	0.0625 A	75 V	1200 Ω	4.69 W

Component	Current	Voltage	Resistance	Power
Source	0.139 A	120 V		16.64 W
R_1	0.096 A	120 V	1250 Ω	11.52 W
R_2	0.032 A	120 V	3750 Ω	3.84 W
R_3	0.0107 A	120 V	11250 Ω	1.28 W

Component	Current	Voltage	Resistance	Power
Source	2.32 A	0.16 V		0.3715 W
R_1	1.45 A	0.16 V	0.110 Ω	0.2327 W
R_2	0.582 A	0.16 V	0.275 Ω	0.0931 W
R_3	0.286 A	0.16 V	0.560 Ω	0.0457 W