


Exam Review - Problem Set 3

$$① \quad I = \frac{V}{R} = \frac{1.5}{3.5} = \boxed{0.43 \text{ A}}$$

$$② \quad V = IR = (6.25)(17.6) = \boxed{110 \text{ V}}$$

③

a)

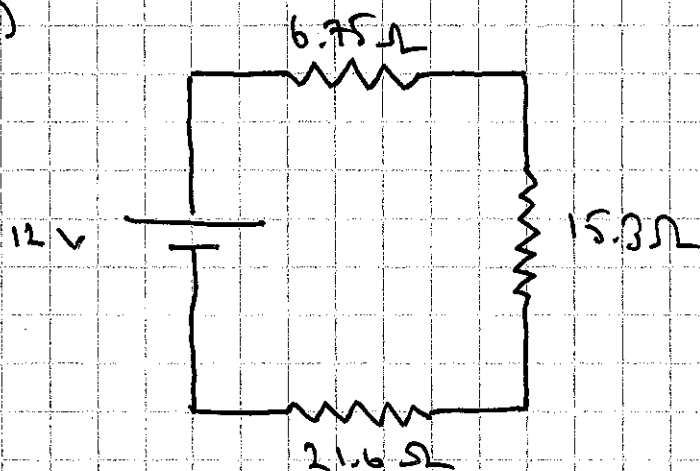

$$b) \quad R_{eq} = 6.75 + 15.3 + 21.6 = \boxed{43.65 \Omega}$$

$$c) \quad I = \frac{V}{R_{eq}} = \frac{12}{43.65} = \boxed{0.275 \text{ A}}$$

④

$$a) \quad R_{eq} = 12 + 12 + 12 = \boxed{36 \Omega}$$


$$b) \quad \frac{1}{R} = \frac{1}{12} + \frac{1}{12} + \frac{1}{12}$$

$$\frac{1}{R} = \frac{3}{12}$$


$$R = \frac{12}{3} = \boxed{4 \Omega}$$

4)

c) Series

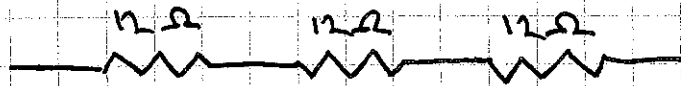

Parallel

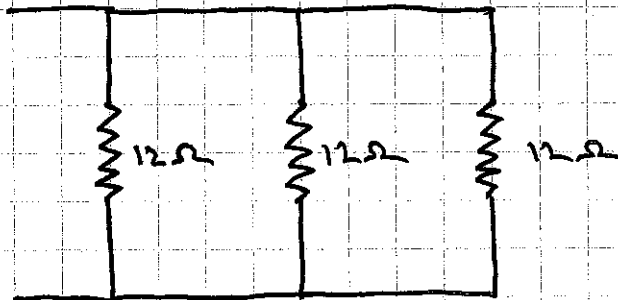

5)

a) $R = \frac{V}{I} = \frac{7.50}{0.50} = \boxed{15\ \Omega}$


b) $A = \pi r^2 = \pi (2 \times 10^{-3})^2 = 3.14 \times 10^{-6}\ \text{m}^2$

$$R = \rho \frac{L}{A}$$

$$\rho = \frac{RA}{L} = \frac{(15)(3.14 \times 10^{-6})}{6.24} = \boxed{7.55 \times 10^{-6}\ \Omega \cdot \text{m}}$$

6)

a)

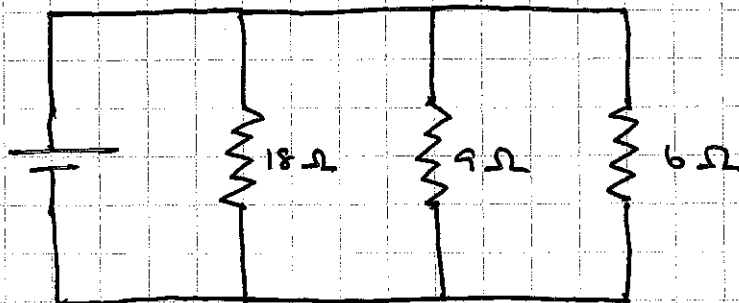

continues on next page

6) a) continued

$$\frac{1}{R} = \frac{1}{18} + \frac{1}{9} + \frac{1}{6}$$
$$= \frac{1}{18} + \frac{2}{18} + \frac{3}{18}$$

$$\frac{1}{R} = \frac{6}{18}$$

$$R = \frac{18}{6} = \boxed{3 \Omega}$$

b) 9 Ω Resistor

$$V = IR = (4)(9) = 36 \text{ V}$$

∴ Battery = $\boxed{36 \text{ V}}$ (all are in parallel, so all have same voltage)


c) 18 Ω

$$I = \frac{V}{R} = \frac{36}{18} = \boxed{2 \text{ A}}$$

6 Ω

$$I = \frac{V}{R} = \frac{36}{6} = \boxed{6 \text{ A}}$$

②

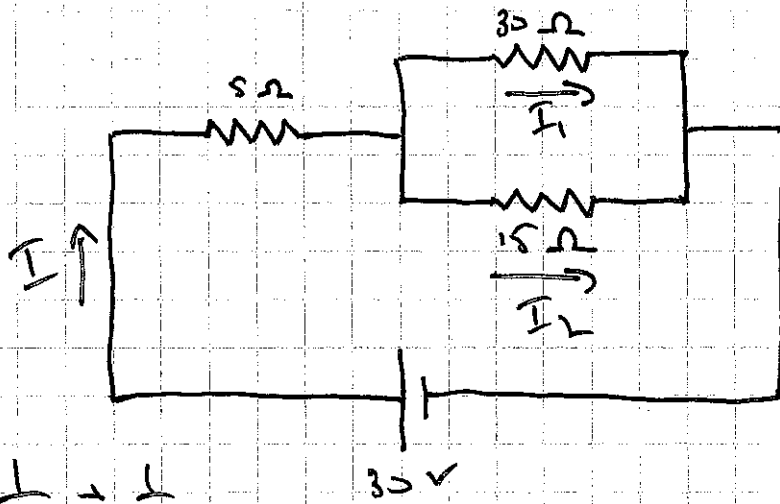


$$R_{T1} = \frac{1}{\frac{1}{30}} = \frac{1}{15}$$


$$R_{T2} = \frac{1}{\frac{1}{30} + \frac{2}{30}}$$

$$R_{T3} = \frac{3}{30}$$

$$R = \frac{30}{3} = 10 \Omega$$

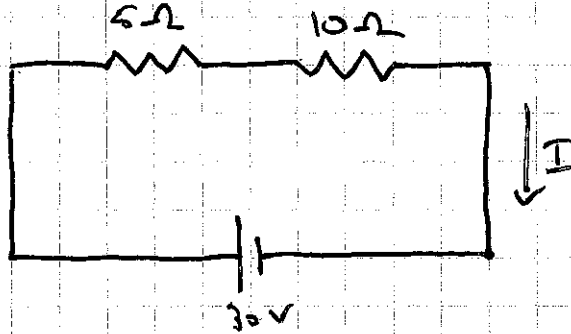

$$R = 5 + 10 = 15 \Omega$$

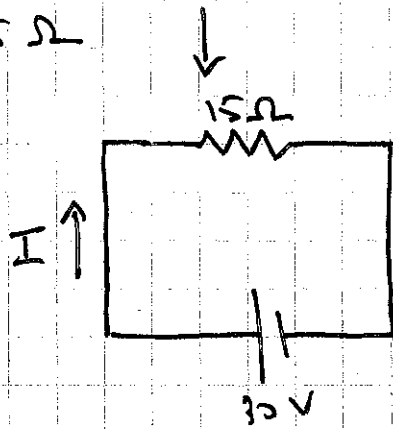

$$I = \frac{V}{R} = \frac{30}{15} = 2 \text{ A}$$

$$V_5 = IR = (2)(5) = 10 \text{ V}$$

$$V_{10} = 30 - V_5 = 30 - 10 = 20 \text{ V}$$

$$I_2 = \frac{V}{R} = \frac{20}{15} = 1.33 \text{ A}$$

$$I_1 = \frac{V}{R} = \frac{20}{30} = 0.67 \text{ A}$$

$$\left. \begin{matrix} V_{30} = 20 \text{ V} \\ V_{15} = 20 \text{ V} \end{matrix} \right\} \text{ both are } = V_{10}$$

8

$$V_5 = V_4$$

$$\therefore V_5 = 4 \text{ V}$$

$$R_5 = \frac{V_5}{I_5} = \frac{4}{1} = 4 \Omega$$

$$I_4 + I_5 = I_{\text{total}}$$

$$I_4 + 1 = 2$$

$$I_4 = 1 \text{ A}$$

$$R_4 = \frac{V_4}{I_4} = \frac{4}{1} = 4 \Omega$$

$$I_1 + I_2 = I_{\text{total}}$$

$$I_1 + 1.5 = 2$$

$$I_1 = 0.5 \text{ A}$$

$$I_2 = I_1 = 0.5 \text{ A}$$

$$I_0 = I_{\text{total}} = 2 \text{ A}$$

$$V_1 = I_1 R_1$$

$$= (0.5)(5)$$

$$V_1 = 2.5 \text{ V}$$

cont in ves on next page

8)

$$R_1 = \frac{V_1}{I_1} = \frac{2.5}{0.5} = 5 \Omega$$

$$V_3 = V_1 + V_2 = 2.5 + 3.5 = 6V$$

$$R_3 = \frac{V_3}{I_3} = \frac{6}{3} = 2 \Omega$$

$$V_6 = I_6 R_6 = (2)(2) = 4V$$

$$V_{source} = V_3 + V_4 + V_6$$

$$= 6 + 4 + 4$$

$$V_{source} = 14V$$

$$R_{eq} = \frac{V_{source}}{I_{source}} = \frac{14}{2} = 7 \Omega$$

	V	I	P
Source	14	2	28
R1	2.5	0.5	1.25
R2	3.5	0.5	1.75
R3	6	3	18
R4	4	2	8
R5	4	2	8
R6	4	2	8

$$\textcircled{9} \quad V = -N \frac{\Delta \Phi}{\Delta t}$$

$$= - (325) \frac{(1.15 \times 10^{-5})}{0.001}$$

$$V = \boxed{-3.74 \text{ V}}$$

$$\textcircled{10} \quad A = \pi r^2 = \pi (0.1)^2 = 0.0314 \text{ m}^2$$

$$V = -N \frac{\Delta \Phi}{\Delta t}$$

$$= - (1) \left[0 - \frac{(0.6)(0.0314)}{0.1} \right]$$

$$V = \boxed{0.188 \text{ V}}$$

- $\textcircled{11}$
- increasing R will decrease I
 - the field of the outer loop (Primary Field) is out of the page
 - flux is decreasing (since B is decreasing, since I is decreasing)
 - \therefore secondary field is also out of the page
 - \therefore induced current is counterclockwise

12

$$V = vBL$$

$$= (0.15 \text{ m/s})(0.8 \text{ T})(0.12 \text{ m})$$

$$V = \boxed{0.0144 \text{ V}}$$

13

$$\frac{Z_p}{Z_s} = \frac{V_s}{V_p}$$

$$\frac{Z_p}{Z_s} = \frac{2400}{120}$$

$$Z_p = 37 \frac{(2400)}{120} = \boxed{1500}$$

14

$$a) \frac{V_p}{V_s} = \frac{Z_p}{Z_s}$$

$$\frac{V_p}{24} = \frac{120}{1500}$$

$$V_s = \frac{120}{1500} = \boxed{24 \text{ V}}$$

$$b) I = \frac{V}{R}$$

$$= \frac{24}{15}$$

$$I = \boxed{1.6 \text{ A}}$$

14)

$$c) P = IV$$
$$= (1.6)(24)$$

$$P = \boxed{38.4 \text{ W}}$$

$$d) \frac{I_p}{I_s} = \frac{Z_s}{Z_p}$$

$$\frac{I_p}{1.6} = \frac{5}{5}$$

$$I_p = \frac{1.6}{5} = \boxed{0.32 \text{ A}}$$