

Electric Circuits Review

3.1 Electric Circuits

Be able to:

- define current
- solve problems for current, charge, and time
- relate conventional current direction to the electron flow in a conductor
- solve problems involving Ohm's law
- describe the factors that affect the resistance of a material
- solve resistivity problems
- calculate the power dissipated in a load
- draw schematics of simple circuits
- construct simple circuits from schematic diagrams
- demonstrate the correct placement of ammeters and voltmeters in simple circuits
- calculate equivalent resistance for series, parallel, and combined networks
- calculate the resistance, current, voltage, and power for series, parallel, and combined networks


Problems

1. Define electric current.
2. A portable compact disc player is designed to play for 2 hours on a fully charged battery pack. If the battery pack provides a total of 180 C of charge, how much current does the player use in operating? (0.025 A)
3. A CD-ROM drive in a laptop computer uses a current of 0.27 A . In one minute, how many electrons pass through the device? (1.01×10^{20})
4. A toaster has a resistance of $14\ \Omega$ and is plugged into a 120 V outlet. What is the current in the toaster? (8.57 A)
5. A battery charger is connected to a dead battery and delivers a current of 6 A for 5 hours, keeping the voltage across the battery terminals at 12 V in the process. How much energy is delivered to the battery? (1296000 J)
6. The resistance of a bagel toaster is $14\ \Omega$. To prepare a bagel, the toaster is operated for one minute from a 120 V outlet. How much energy is delivered to the toaster? (61714 J)
7. Explain the difference between conventional current direction and the direction of electron flow in a conductor.
8. Identify four factors affecting the resistance of a material. Explain how each affects the resistance.
9. High voltage power lines are a familiar sight throughout the country. The aluminum wire used for some of these lines has a cross sectional area of $4.9 \times 10^{-4}\text{ m}^2$. What is the resistance of ten kilometers of this wire? ($0.54\ \Omega$)
10. The filament in an incandescent light bulb is made from tungsten. The radius of the tungsten wire is 0.045 mm . If the bulb is to be plugged into a 120 V outlet and is to draw a current of 1.24 A , how long must the wire be? (10.9 m)
11. Two conducting wires of the same material are to have the same resistance. One wire is 20 m long and 0.40 mm in diameter. If the other wire is 0.30 mm in diameter, how long should it be? (11.25 m)
12. Two cylindrical bars, each with a diameter of 2.30 cm , are welded together end to end. One of the original bars is copper and is 0.470 m long. The other bar is iron and is 0.125 m long. What is the resistance between the ends of the two bars? ($4.87 \times 10^{-5}\ \Omega$)


13. Draw a schematic that consists of:
- three 1.5 V cells connected in parallel
 - a switch
 - two light bulbs connected in series
 - two light bulbs connected in parallel
 - a voltmeter to measure the voltage drop across one of the light bulbs
 - an ammeter to measure the current provided by the battery
14. Draw a schematic that consists of:
- a 6.0 V source
 - a switch
 - two lamps in series, in parallel with a single lamp
 - an ammeter to measure the current through one of the lamps in parallel
 - a voltmeter to measure the voltage drop across all three lamps
15. Three resistors, $50\ \Omega$, $90\ \Omega$, and $150\ \Omega$, are connected in series, and a 1.02 A current passes through them. What is
- a) the equivalent resistance? ($290\ \Omega$)
 - b) the potential difference across the three resistors? (295.8 V)
16. A $45\ \Omega$ resistor and an $18\ \Omega$ resistor are connected in series across a 12 V battery. What is the voltage across
- a) the $45\ \Omega$ resistor? (8.57 V)
 - b) the $18\ \Omega$ resistor? (3.43 V)
17. The current in a series circuit is 24.0 A . When an additional $12\ \Omega$ resistor is inserted in series, the current drops to 18.0 A . What is the resistance of the original circuit?
($36\ \Omega$)
18. A $4\ \Omega$ loudspeaker and an $8\ \Omega$ loudspeaker are connected in parallel across the terminals of an amplifier. Assuming the speakers behave as resistors, determine the equivalent resistance of the two speakers. ($2.67\ \Omega$)
19. Two resistors, $42\ \Omega$ and $64\ \Omega$ are connected in parallel. The current through the $64\ \Omega$ resistor is 3.00 A .
- a) Determine the current in the other resistor. (4.57 A)
 - b) What is the total power consumed by the two resistors? (1454 W)

20. Three resistors of $100\ \Omega$, $47\ \Omega$, and $33\ \Omega$ are joined together in parallel. What is the equivalent resistance? ($16.2\ \Omega$)

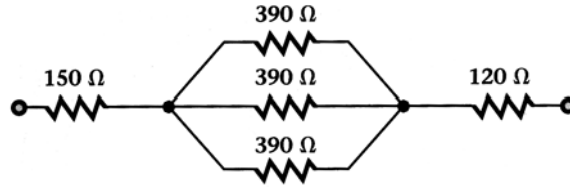
21. Find the equivalent resistance of the network shown below. ($400\ \Omega$)



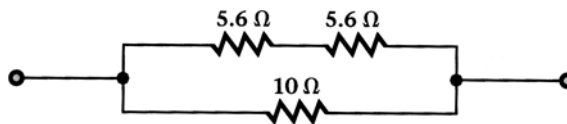22. Find the equivalent resistance of the network shown below. ($5.3\ \Omega$)



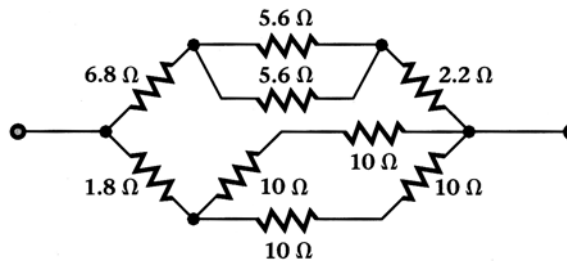23. Find the equivalent resistance of the network shown below. ($5.9\ \Omega$)




24. An elevator in a 20-story building is used to raise a $7200\ N$ load $50\ m$. How much will it cost to raise the load if electricity costs $\$0.078 / kWh$? Assume that the elevator system is 50% efficient – that is, that the energy expended in raising the load is half of the total energy consumed. (1.6 cents)

25. A $1500\ \Omega$ resistor is rated at $2.0\ W$ maximum power capacity.

a) What is the maximum voltage that can be applied across the resistor without exceeding its maximum power rating? ($55\ V$)

b) What is the maximum current? ($0.037\ A$)

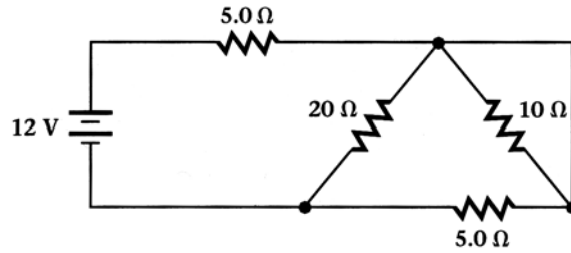26. What is the current through (a) the $10\ \Omega$ resistor and (b) the $20\ \Omega$ resistor in the diagram below? ($0\ \text{A}$, $0.27\ \text{A}$)



27. Two resistors are connected in series across an ideal $12.0\ \text{V}$ battery. Resistor A has a value of $24.0\ \Omega$ and the potential difference across resistor B is $3.60\ \text{V}$.

- What is the potential difference across A ? ($8.4\ \text{V}$)
- What is the current in the resistors? ($0.35\ \text{A}$)
- What is the resistance of B ? ($10.3\ \Omega$)
- What is the total power dissipated in the circuit? ($4.2\ \text{W}$)

28. Three resistors are joined together across a $24.0\ \text{V}$ battery, as shown below. The voltage drop across resistor R_1 is $8.0\ \text{V}$, the current through resistor R_2 is $0.20\ \text{A}$, and the power dissipated in resistor R_3 is $2.56\ \text{W}$.

- What is the value of each resistor? ($R_1 = 22.2\ \Omega$, $R_2 = 80\ \Omega$, $R_3 = 100\ \Omega$)
- What is the current through each resistor? ($I_1 = 0.36\ \text{A}$, $I_2 = 0.2\ \text{A}$, $I_3 = 0.16\ \text{A}$)
- What is the power dissipated in each resistor? ($P_1 = 2.88\ \text{W}$, $P_2 = 3.2\ \text{W}$, $P_3 = 2.56\ \text{W}$)
- Find the total resistance of the network. ($66.7\ \Omega$)
- Find the current drawn from the battery. ($0.36\ \text{A}$)
- Find the total power used by the circuit. ($8.64\ \text{W}$)

